

Solution 1.1

Answering machine

Alarm clock

Automatic door

Automatic lights

ATM

Automobile:

 Engine controller

 Temperature control

 ABS

 Electronic dash

 Navigation system

Automotive tune-up equipment

Baggage scanner

Bar code scanner

NiCad/Lithium Ion battery chargers

Cable/DSL Modems and routers

Calculator

Camcorder

Carbon monoxide detector

Cash register

CD and DVD players

Ceiling fan (remote)

Cellular phones

Coffee maker

Compass

Copy machine

Cordless phone

Depth finder

Digital Camera

Digital watch

Digital voice recorder

Digital scale

Digital thermometer

Electronic dart board

Electric guitar

Electronic door bell

Electronic gas pump

Elevator

Exercise machine

Fax machine

Fish finder

Garage door opener

Solution continued on the next page...

GPS
Hearing aid
Invisible dog fences
Laser pointer
LCD projector
Light dimmer
Keyboard synthesizer
Keyless entry system
Laboratory instruments
Metal detector
Microwave oven
Model airplanes
MP3 player
Musical greeting cards
Musical tuner
Pagers
Personal computer
Personal planner/organizer (PDA)
Radar detector
Broadcast Radio (AM/FM/Shortwave)
Razor
Satellite radio receiver
Security systems
Sewing machine
Smoke detector
Sprinkler system
Stereo system
 Amplifier
 CD/DVD player
 Receiver
 Tape player
Stud sensor
Talking toys
Telephone
Telescope controller
Thermostats
Toy robots
Traffic light controller
TV receiver & remote control
Variable speed appliances
 Blender
 Drill
 Mixer
 Food processor
 Fan

Solution continued on the next page...

Copyright © McGraw-Hill Education. This is proprietary material solely for authorized instructor use. Not authorized for sale or distribution in any manner. This document may not be copied, scanned, duplicated, forwarded, distributed, or posted on a website, in whole or part.

Vending machines
Video game controllers
Wireless headphones & speakers
Wireless thermometer
Workstations

Electromechanical Appliances*

Air conditioning and heating systems
Clothes washer and dryer
Dish washer
Electrical timer
Iron, vacuum cleaner, toaster
Oven, refrigerator, stove, etc.

*These appliances are historically based only upon on-off (bang-bang) control. However, most high end versions of these appliances have now added sophisticated electronic control.

Solution 1.2

$$N = 1327 \times 10^{(2020-1970)/6.52} = 61.9 \times 10^9 \text{ transistors/chip}$$

Solution 1.3

$$N = (2.233 \times 10^9) \times 10^{(2021-2014)/10.1} = 11.0 \times 10^9 \text{ Transistors/Chip}$$

Solution 1.4

$$B = 19.97 \times 10^{0.1997(2021-1960)} = 30.3 \times 10^{12} = 30.3 \text{ Tb/chip}$$

Solution 1.5

(a)

$$\frac{B_2}{B_1} = \frac{19.97x10^{0.1977(Y_2-1960)}}{19.97x10^{0.1977(Y_1-1960)}} = 10^{0.1977(Y_2-Y_1)} \text{ so } 2 = 10^{0.1977(Y_2-Y_1)}$$

$$Y_2 - Y_1 = \frac{\log 2}{0.1977} = 1.52 \text{ years}$$

(b) $Y_2 - Y_1 = \frac{\log 10}{0.1977} = 5.06 \text{ years}$

Solution 1.6

$$\frac{N_2}{N_1} = \frac{1327x10^{(Y_2-1970)/6.52}}{1327x10^{(Y_1-1970)/6.52}} = 10^{(Y_2-Y_1)/6.52}$$

(a) $Y_2 - Y_1 = 6.52 \log 2 = 1.96$ years

(b) $Y_2 - Y_1 = 6.52 \log 10 = 6.52$ years

Solution 1.7

$$\frac{N_2}{N_1} = \frac{(2.233 \times 10^9) x 10^{(Y_2 - 2014)/10.1}}{(2.233 \times 10^9) x 10^{(Y_1 - 2014)/10.1}} = 10^{(Y_2 - Y_1)/10.1}$$

(a) $Y_2 - Y_1 = 10.1 \log 2 = 3.07$ years

(b) $Y_2 - Y_1 = 10.1 \log 10 = 10.1$ years

Solution 1.8

$$F = 8.00 \times 10^{-0.05806(2020-1970)} \mu m = 10 \text{ nm} .$$

Although this distance corresponds to the diameter of only a few atoms, ITRS projections are on track to produce feature sizes in this range. See the Intel website for example.

Solution 1.9

$$P = (268 \times 10^6 \text{ tubes})(1.5 \text{ W/tube}) = 402 \text{ MW!} \quad I = \frac{4.02 \times 10^8 \text{ W}}{220 \text{ V}} = 1.83 \text{ MA!}$$

$$V = (268 \times 10^6 \text{ tubes})(80 \text{ cm}^3 / \text{tube}) = 21.4 \times 10^9 \text{ cm}^3 = 21400 \text{ m}^3$$

Solution 1.10

D, D, A, A, D, A, A, D, A, D, A

Solution 1.11

$$V_{LSB} = \frac{5V}{2^8 \text{ bits}} = \frac{5V}{256 \text{ bits}} = 19.53 \frac{\text{mV}}{\text{bit}} \quad \text{and} \quad \frac{3.06V}{19.53 \frac{\text{mV}}{\text{bit}}} = 156.7 \text{ bits} \rightarrow 157 \text{ LSB}$$

$$157_{10} = (128 + 16 + 8 + 4 + 1)_{10} = 10011101_2$$

Solution 1.12

$$V_{LSB} = \frac{2.5V}{2^{10} \text{ bits}} = \frac{2.5V}{1024 \text{ bits}} = 2.441 \frac{mV}{\text{bit}}$$

$$0101100110_2 = (2^8 + 2^6 + 2^5 + 2^2 + 2^1)_{10} = 358_{10} \quad V_o = 358 \left(\frac{2.5V}{1024} \right) = 0.874 \text{ V}$$

Solution 1.13

$$V_{LSB} = \frac{10V}{2^{12} \text{ bits}} = \frac{10V}{4096 \text{ bits}} = 2.441 \text{ mV}$$

$$V_{MSB} = \frac{10V}{2} = 5.000 \text{ V}$$

$$100100101001_2 = 2^{11} + 2^8 + 2^5 + 2^3 + 2^0 = 2345_{10} \quad V_O = 2345(2.441 \text{ mV}) = 5.724 \text{ V}$$

Solution 1.14

$$V_{LSB} = \frac{10V}{2^{15} \text{ bits}} = 0.3052 \frac{\text{mV}}{\text{bit}} \quad \text{and} \quad \frac{6.89V}{10V} (2^{15} \text{ bits}) = 22577 \text{ bits}$$

$$22577_{10} = (16384 + 4096 + 2048 + 32 + 16 + 1)_{10}$$

$$22577_{10} = 101100000110001_2$$

Solution 1.15

(a) A 4 digit readout ranges from 0000 to 2000 and has a resolution of 1 part in 2,000. The number of bits must satisfy $2^B \geq 2,000$ where B is the number of bits. Here B = 11 bits.

(b) $2^B \geq 10^6$ yields B = 20 bits.

Solution 1.16

$$V_{LSB} = \frac{5.12V}{2^{14} \text{ bits}} = \frac{5.12V}{16384 \text{ bits}} = 0.3125 \frac{mV}{\text{bit}} \quad \text{and} \quad V_O = (10101110111010_2) V_{LSB} \pm \frac{V_{LSB}}{2}$$

$$V_O = (2^{13} + 2^{11} + 2^9 + 2^8 + 2^7 + 2^5 + 2^4 + 2^3 + 2^1)_{10} 0.3125mV \pm 0.1625mV$$

$$V_O = 3.49813 \pm 0.0001625 \quad \text{or} \quad 3.49798V \leq V_O \leq 3.49829V$$

Solution 1.17

$I_B = \text{dc component} = 7.50 \text{ mA}$, $i_b = \text{signal component} = 0.003 \cos(1000t) \text{ A}$

Solution 1.18

$$V_{GS} = 2.5 \text{ V}, \quad v_{gs} = 0.5u(t-1) + 0.1 \cos 2000\pi t \text{ Volts}$$


Solution 1.19

$$v_{CE} = [5 + 2 \cos (5000t)] \text{ V}$$

Solution 1.20

$$v_{DS} = [5 + 2 \sin (2500t) + 4 \sin (1000t)] \text{ V}$$

Solution 1.21

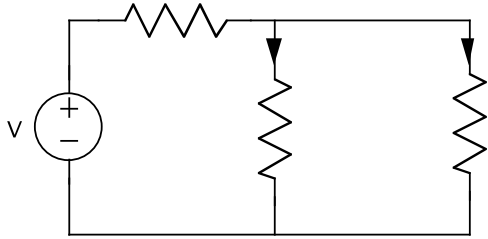

$V = 1 \text{ V}$, $R_1 = 24 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$ and $R_3 = 11 \text{ k}\Omega$.


$$V_1 = 1V \frac{24k\Omega}{24k\Omega + (30k\Omega \parallel 11k\Omega)} = 0.749 \text{ V} \quad V_2 = 1V \frac{30k\Omega \parallel 11k\Omega}{24k\Omega + (30k\Omega \parallel 11k\Omega)} = 0.251 \text{ V}$$

Checking: $V_1 + V_2 = 0.749 + 0.251 = 1.00 \text{ V}$ which is correct.

$$I_1 = \frac{1V}{24k\Omega + (30k\Omega \parallel 11k\Omega)} = 31.2 \mu\text{A} \quad I_2 = I_1 \frac{R_3}{R_2 + R_3} = (31.2\mu\text{A}) \frac{11k\Omega}{30k\Omega + 11k\Omega} = 8.37 \mu\text{A}$$

$$I_3 = I_1 \frac{R_2}{R_2 + R_3} = (31.2\mu\text{A}) \frac{30k\Omega}{30k\Omega + 11k\Omega} = 22.8 \mu\text{A} \quad \text{Checking: } I_2 + I_3 = 31.2 \mu\text{A}$$

Solution 1.22

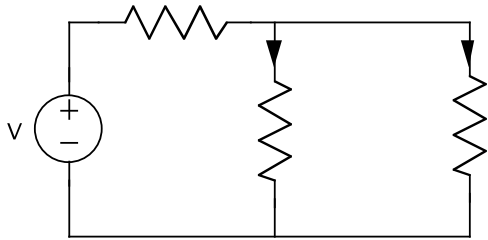

$V = 8 \text{ V}$, $R_1 = 30 \text{ k}\Omega$, $R_2 = 24 \text{ k}\Omega$ and $R_3 = 15 \text{ k}\Omega$.

$$V_1 = 8V \frac{30k\Omega}{30k\Omega + (24k\Omega \parallel 15k\Omega)} = 8V \frac{30k\Omega}{30k\Omega + 9.23k\Omega} = 6.12 \text{ V}$$

$$V_2 = 8V \frac{24k\Omega \parallel 15k\Omega}{30k\Omega + (24k\Omega \parallel 15k\Omega)} = 1.88 \text{ V} \quad \text{Checking: } 6.12 + 1.88 = 8.00 \text{ V}$$

$$I_2 = I_1 \frac{R_3}{R_2 + R_3} = \left(\frac{8V}{30k\Omega + 9.23k\Omega} \right) \frac{15k\Omega}{24k\Omega + 15k\Omega} = 78.4 \mu\text{A}$$

$$I_3 = I_1 \frac{R_2}{R_2 + R_3} = \left(\frac{8V}{30k\Omega + 9.23k\Omega} \right) \frac{24k\Omega}{24k\Omega + 15k\Omega} = 125 \mu\text{A}$$

$$\text{Checking: } I_1 = \frac{8V}{30k\Omega + 9.23k\Omega} = 204 \mu\text{A} \quad \text{and} \quad I_1 = I_2 + I_3$$

Solution 1.23

$$I_2 = 200\mu\text{A} \left(\frac{150k\Omega}{150k\Omega + 150k\Omega} \right) = 100 \mu\text{A} \quad I_3 = 200\mu\text{A} \left(\frac{150k\Omega}{150k\Omega + 150k\Omega} \right) = 100 \mu\text{A}$$

$$V_3 = 200\mu\text{A} (150k\Omega \parallel 150k\Omega) \left(\frac{82k\Omega}{68k\Omega + 82k\Omega} \right) = 8.2V$$

$$\text{Checking: } I_1 + I_2 = 200 \mu\text{A} \quad \text{and} \quad I_2 R_2 = 100\mu\text{A} (82k\Omega) = 8.2 V$$

Solution 1.24

$$I_1 = 4mA \frac{(3.9k\Omega + 5.6k\Omega)}{(3.9k\Omega + 5.6k\Omega) + 2.4k\Omega} = 3.19 \text{ mA} \quad I_2 = 4mA \frac{2.4k\Omega}{9.5k\Omega + 2.4k\Omega} = 0.807 \text{ mA}$$

$$V_3 = 4mA (2.4k\Omega \parallel 9.5k\Omega) \frac{5.6k\Omega}{3.9k\Omega + 5.6k\Omega} = 4.52 \text{ V}$$


$$\text{Checking: } I_1 + I_2 = 4.00 \text{ mA} \quad \text{and} \quad I_2 R_3 = 0.807mA (5.6k\Omega) = 4.52 \text{ V}$$

Solution 1.25

Summing currents at the open circuited output node yields:

$$\frac{v}{10^4} + 0.025v = 0 \text{ so } v = 0 \text{ and } v_{th} = v_i - v = v_i$$

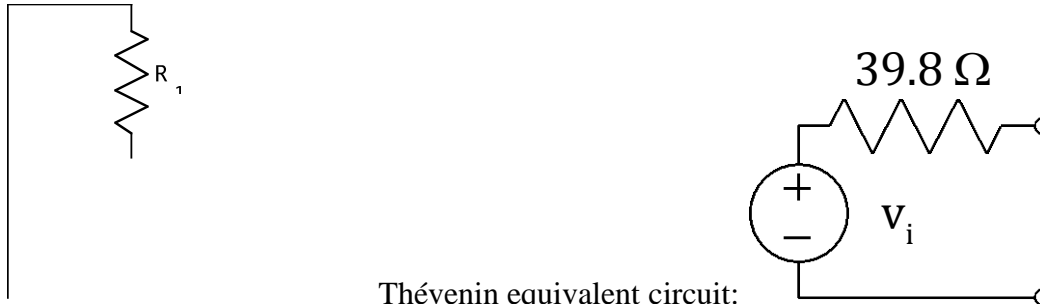To find the Thévenin equivalent resistance, we apply a test source to the output with v_i set to zero:




Thévenin equivalent circuit:

Summing currents at the output node:


$$i_x = -\frac{v}{R_1} - g_m v = 0 \text{ but } v = -v_x$$

$$i_x = \frac{v_x}{R_1} + g_m v_x = 0 \quad R_{th} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{R_1} + g_m} = \frac{1}{\frac{1}{10k\Omega} + 0.025S} = 39.8 \Omega$$

Solution 1.26

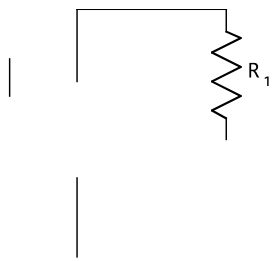


Norton equivalent circuit:

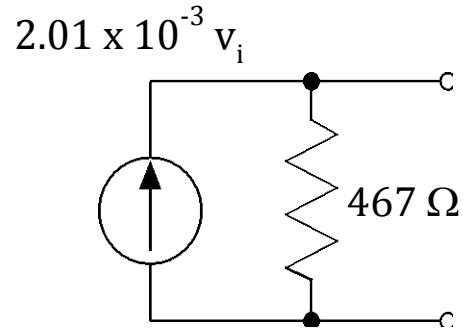

The short circuit current is:

$$i_n = \frac{v}{75k\Omega} + 0.002v \text{ and } v = v_i \rightarrow i_n = \frac{v_i}{75k\Omega} + 0.002v_i = 2.01 \times 10^{-3} v_i$$

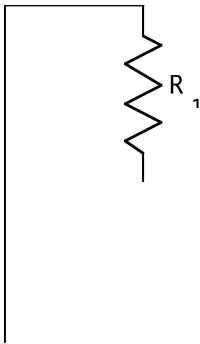To find the Thévenin equivalent resistance, we apply a test source to the output with v_i set to zero:




Summing currents at the output node:


$$i_x = -\frac{v}{R_1} - g_m v = 0 \text{ but } v = -v_x$$

$$i_x = \frac{v_x}{R_1} + g_m v_x = 0 \quad R_{th} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{R_1} + g_m} = \frac{1}{\frac{1}{75k\Omega} + 0.002S} = 467 \Omega$$


Solution 1.27

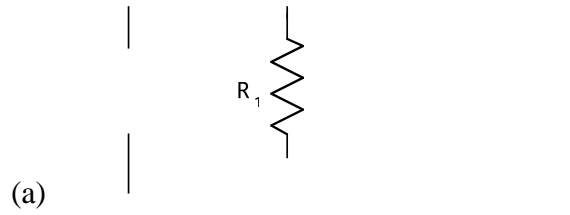

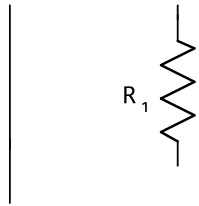
$$i_n = -\beta i \text{ but } i = -\frac{v_i}{R_1} \text{ and } i_n = \frac{\beta}{R_1} v_i = \frac{150}{39k\Omega} v_i = 3.85 \times 10^{-3} v_i$$


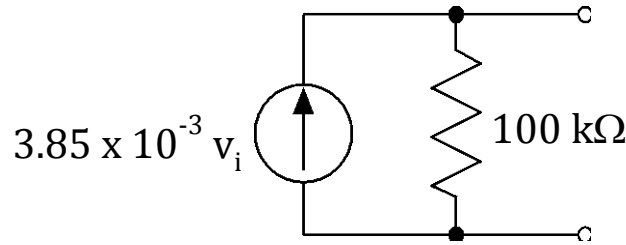
$$R_{th} = \frac{v_x}{i_x} ; i_x = \frac{v_x}{R_2} + \beta i \text{ but } i = 0 \text{ since } v_{R_1} = 0. R_{th} = R_2 = 100 \text{ k}\Omega.$$




Norton equivalent circuit:

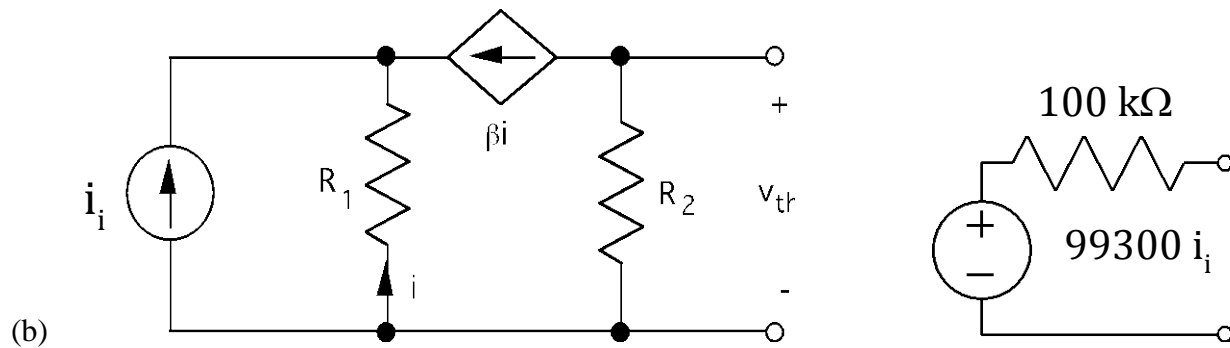


$$v_{th} = v_{oc} = -\beta i R_2 \text{ where } i + \beta i + i_i = 0 \text{ and } v_{th} = R_2 \left(\frac{\beta}{\beta + 1} \right) i_i = 100k\Omega \left(\frac{150}{151} \right) i_i = 99300 i_i$$

R_{th} is found in part (a).


Solution 1.28

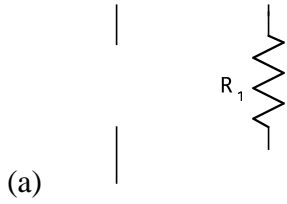
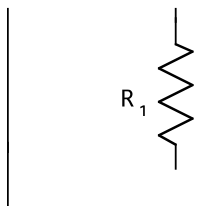
$$v_{th} = v_{oc} = -\beta i R_2 \quad \text{but} \quad i = -\frac{v_i}{R_1} \quad \text{and} \quad v_{th} = \beta v_i \frac{R_2}{R_1} = 120 v_i \frac{56k\Omega}{75k\Omega} = 89.6 v_i$$



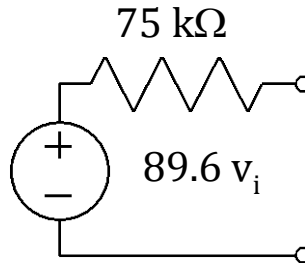
$$R_{th} = \frac{v_x}{i_x} ; \quad i_x = \frac{v_x}{R_2} + \beta i \quad \text{but} \quad i = 0 \quad \text{since} \quad v_{R_1} = 0. \quad R_{th} = R_2 = 75 k\Omega.$$




Thévenin equivalent circuit:

(b)

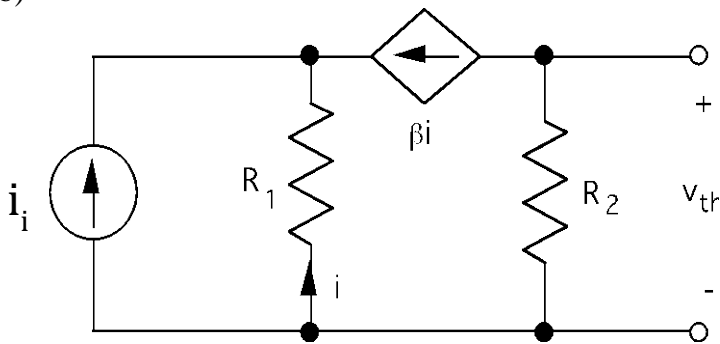


$$v_{th} = v_{oc} = -\beta i R_2 \quad \text{where} \quad i + \beta i + i_i = 0 \quad \text{and} \quad v_{th} = R_2 \left(\frac{\beta}{\beta + 1} \right) i_i = 75k\Omega \left(\frac{120}{121} \right) i_i = 74400 i_i$$

Solution continued on the next page....


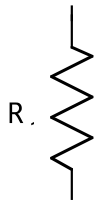

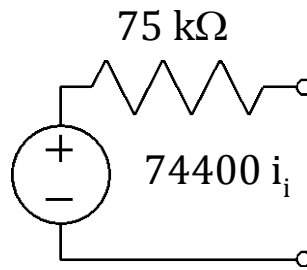
$$R_{th} = \frac{v_x}{i_x} ; \quad i_x = \frac{v_x}{R_2} + \beta i \quad \text{but} \quad i + \beta i = 0 \quad \text{so} \quad i = 0 \quad \text{and} \quad R_{th} = R_2 = 75 \text{ k}\Omega$$



Thévenin equivalent circuit:

Solution 1.29

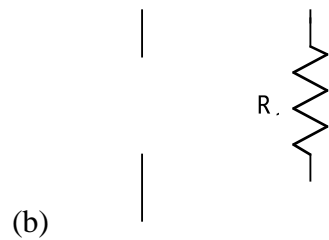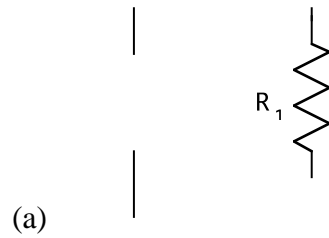

$$(a) \quad i_i = \frac{v_i}{R_1} - \beta i = \frac{v_i}{R_1} + \beta \frac{v_i}{R_1} = v_i \frac{\beta + 1}{R_1} \quad R = \frac{v_i}{i_i} = \frac{R_1}{\beta + 1} = \frac{100k\Omega}{76} = 1.32 \text{ k}\Omega$$

(b) Source is i_i in part (b).

$$v_i = -iR_1 \quad \text{and} \quad i_i = -i - \beta i = -(\beta + 1)i \quad R = \frac{v_i}{i_i} = -\frac{-1}{\beta + 1} R_1 = \frac{100k\Omega}{76} = 1.32 \text{ k}\Omega$$

Solution 1.30

The open circuit voltage is $v_{th} = -g_m v R_2$ where $v = +i_i R_1$.

$$v_{th} = -g_m R_1 R_2 i_i = -(0.0025)(2 \times 10^5)(2 \times 10^6) i_i = 1.0 \times 10^9 i_i$$

For $i_i = 0$, $v = 0$, and $R_{th} = R_2 = 2 \text{ M}\Omega$

Solution 1.31

$$(a) R_{AB} = 10k\Omega + 10k\Omega \parallel \left[10k\Omega + (10k\Omega \parallel 10k\Omega) \right] = 16 k\Omega$$

$$(b) R_{CD} = 10k\Omega \parallel \left[10k\Omega + (10k\Omega \parallel 10k\Omega) \right] = 6 k\Omega$$

$$(c) R_{EF} = 10k\Omega \parallel 10k\Omega \parallel (10k\Omega + 10k\Omega) = 4 k\Omega$$

$$(d) \text{ Terminals B \& D are the same as E \& F. } R_{BD} = 4 k\Omega$$

Solution 1.32

(a) The open-circuit voltage is $v_{th} = 18V \frac{36k\Omega}{82k\Omega + 36k\Omega} = 5.49 V$

The Thevenin equivalent resistance is $R_{th} = 36k\Omega \parallel 82k\Omega = 25.0 k\Omega$

(b) The short-circuit current is $i_n = \frac{18V}{82k\Omega} = 220 \mu A$

The Thevenin equivalent resistance is $R_{th} = 36k\Omega \parallel 82k\Omega = 25.0 k\Omega$

Checking: $i_n R_{th} = 5.49 V$ which equals v_{th} and is correct.

Solution 1.33

(a) The open-circuit voltage is $v_{th} = -9V + I \times 27k\Omega = -9V + \left(\frac{18V}{68k\Omega + 27k\Omega}\right) 27k\Omega = -3.88 V$

The open-circuit voltage is also $v_{th} = +9V - I \times 68k\Omega = -9V + \left(\frac{18V}{68k\Omega + 27k\Omega}\right) 68k\Omega = -3.88 V$

Using voltage division yields $v_{th} = -9V + 18V \left(\frac{27k\Omega}{68k\Omega + 27k\Omega}\right) = -3.88 V$

Using voltage division yields $v_{th} = +9V - 18V \left(\frac{68k\Omega}{68k\Omega + 27k\Omega}\right) = -3.88 V$

The Thevenin equivalent resistance is $R_{th} = 27k\Omega \parallel 68k\Omega = 19.3 k\Omega$

(b) The short-circuit current is $i_n = \frac{9V}{68k\Omega} - \frac{9V}{27k\Omega} = -201 \mu A$


The Thevenin equivalent resistance is $R_{th} = 27k\Omega \parallel 68k\Omega = 19.3 k\Omega$

Checking: $i_n R_{th} = -3.88 V$ which equals v_{th} and is correct.


Solution 1.34

(a) If the $36\text{ k}\Omega$ resistor was shorted, or the $82\text{ k}\Omega$ resistor was open, then the output voltage would be 0. If the $82\text{ k}\Omega$ resistor was shorted, the output would be 18 V (unless the $36\text{ k}\Omega$ resistor was also shorted). (b) If the $68\text{ k}\Omega$ resistor was shorted, or the $27\text{ k}\Omega$ resistor was open, then the output voltage would be $+9\text{ V}$. If the $27\text{ k}\Omega$ resistor was shorted, or the $68\text{ k}\Omega$ resistor was open, the output would be -9 V . Otherwise the voltage would be between -9 and $+9$ volts.

Solution 1.35

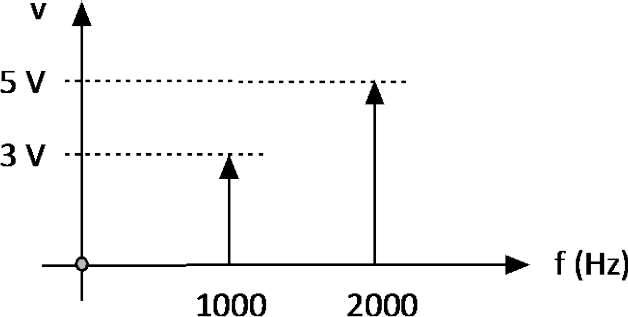


Solution 1.36

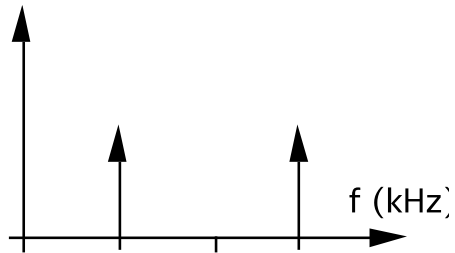

$$v = 4 \sin(20000\pi t) \sin(2000\pi t) = \frac{4}{2} [\cos(20000\pi t + 2000\pi t) + \cos(20000\pi t - 2000\pi t)]$$

$$v = 2 \cos(22000\pi t) + 2 \cos(18000\pi t)$$

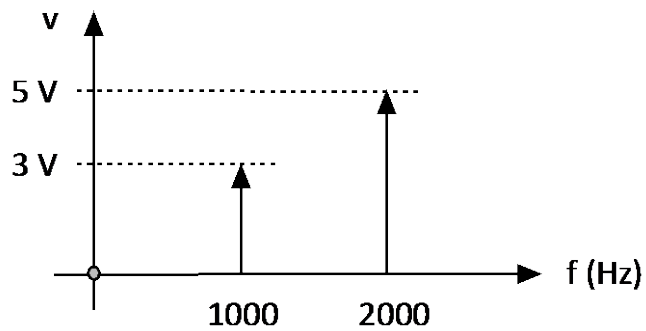

Solution 1.37

$$A = \frac{4 \angle 56^\circ}{10^{-4} \angle 0^\circ} = 4 \times 10^4 \angle 56^\circ \quad |A| = 4 \times 10^4 \quad \angle A = 56^\circ$$

Solution 1.38

$$(a) A = \frac{10^{-1} \angle -12^\circ}{2 \times 10^{-3} \angle 0^\circ} = 50 \angle -12^\circ \quad |A| = 50 \quad \angle A = -12^\circ$$

$$(b) A = \frac{10^{-2} \angle -45^\circ}{10^{-3} \angle 0^\circ} = 10 \angle -45^\circ \quad |A| = 10 \quad \angle A = -45^\circ$$

Solution 1.39

$$(a) A_v = -\frac{R_2}{R_1} = -\frac{560k\Omega}{12k\Omega} = -46.7 \quad (b) A_v = -\frac{360k\Omega}{18k\Omega} = -20.0 \quad (c) A_v = -\frac{62k\Omega}{2k\Omega} = -31.0$$

Solution 1.40

$$v_o(t) = -\frac{R_2}{R_1} v_i(t) = -\frac{7500}{910} (0.01 \sin 750\pi t) = (-82.4 \sin 750\pi t) \text{ mV}$$

$$i_i = \frac{v_i}{R_1} = \frac{0.01V}{910\Omega} = 11.0\mu A \quad \text{and} \quad i_i(t) = (11.0 \sin 750\pi t) \mu A$$

Solution 1.41

Since the voltage across the op amp input terminals must be zero, $v_- = v_+$ and $v_o = v_i$.

Therefore $A_v = 1$.

Solution 1.42

Since the voltage across the op amp input terminals must be zero, $v_- = v_+ = v_i$. Also, $i_- = 0$.

$$\frac{v_- - v_o}{R_2} + i_- + \frac{v_-}{R_1} = 0 \quad \text{or} \quad \frac{v_i - v_o}{R_2} + \frac{v_i}{R_1} = 0 \quad \text{and} \quad A_v = \frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$

Solution 1.43

Writing a nodal equation at the inverting input terminal of the op amp gives

$$\frac{v_1 - v_-}{R_1} + \frac{v_2 - v_-}{R_2} = i_- + \frac{v_- - v_o}{R_3} \quad \text{but } v_- = v_+ = 0 \quad \text{and } i_- = 0$$

$$v_o = -\frac{R_3}{R_1}v_1 - \frac{R_3}{R_2}v_2 = (-0.255\sin 3770t - 0.250\sin 10000t) \text{ volts}$$

Solution 1.44

$$v_O = -V_{REF} \left(\frac{b_1}{2} + \frac{b_2}{4} + \frac{b_3}{8} \right)$$

$$(a) v_O = -5 \left(\frac{0}{2} + \frac{1}{4} + \frac{1}{8} \right) = -1.875V \quad (b) v_O = -5 \left(\frac{1}{2} + \frac{0}{4} + \frac{0}{8} \right) = -2.500V$$


$b_1b_2b_3$	v_O (V)
000	0
001	-0.625
010	-1.250
011	-1.875
100	-2.500
101	-3.125
110	-3.750
111	-4.375

Solution 1.45

Low-pass amplifier


Amplitude

Solution 1.46

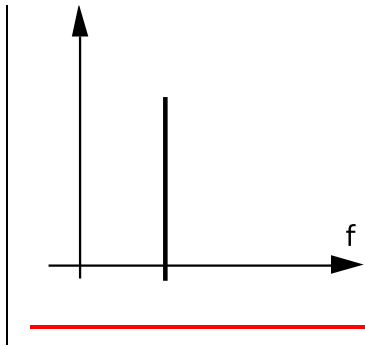

Solution 1.46

High-pass amplifier

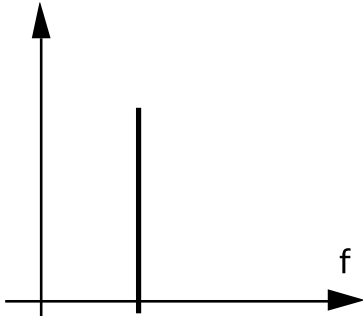

Solution 1.48**Refers to Prob. 1.45**

$$v_o(t) = 10x5\sin(2000\pi t) + 10x3\cos(8000\pi t) + 0x3\cos(15000\pi t)$$

$$v_o(t) = [50\sin(2000\pi t) + 30\cos(8000\pi t)] \text{ volts}$$

Solution 1.49

$$v_o(t) = 20 \times 0.5 \sin(2500\pi t) + 20 \times 0.75 \cos(8000\pi t) + 0 \times 0.6 \cos(12000\pi t)$$


$$v_o(t) = [10.0 \sin(2500\pi t) + 15.0 \cos(8000\pi t)] \text{ volts}$$

Solution 1.50


The gain is zero at each frequency: $v_o(t) = 0$.

Solution 1.51
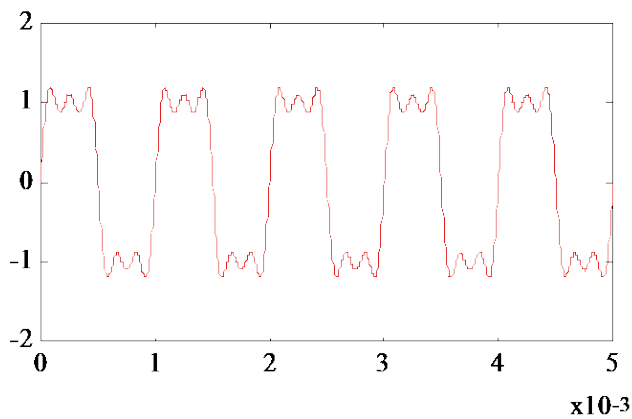
```
t=linspace(0,.005,1000);  
w=2*pi*1000;  
v=(4/pi)*(sin(w*t)+sin(3*w*t)/3+sin(5*w*t)/5);  
v1=5*v;  
v2=5*(4/pi)*sin(w*t);  
v3=(4/pi)*(5*sin(w*t)+3*sin(3*w*t)/3+sin(5*w*t)/5);  
plot(t,v)  
plot(t,v1)  
plot(t,v2)  
plot(t,v3)
```




(a)

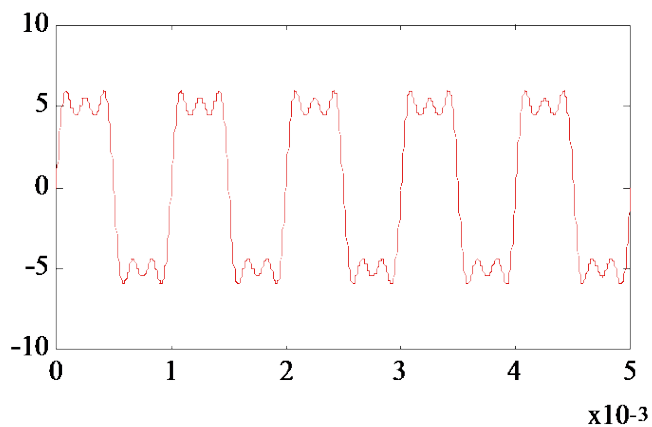


(b)

Solution continued on the next page....

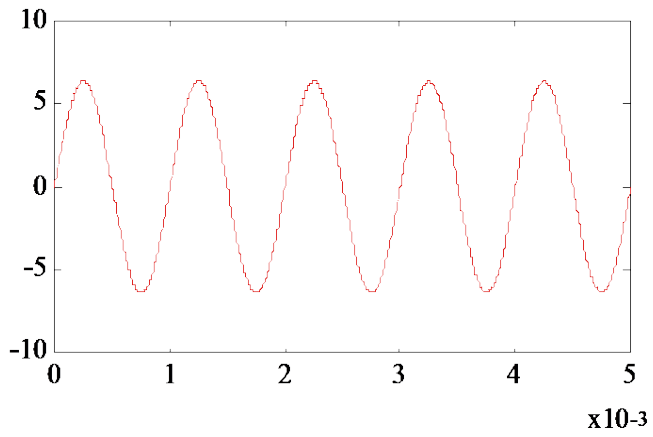

(c)

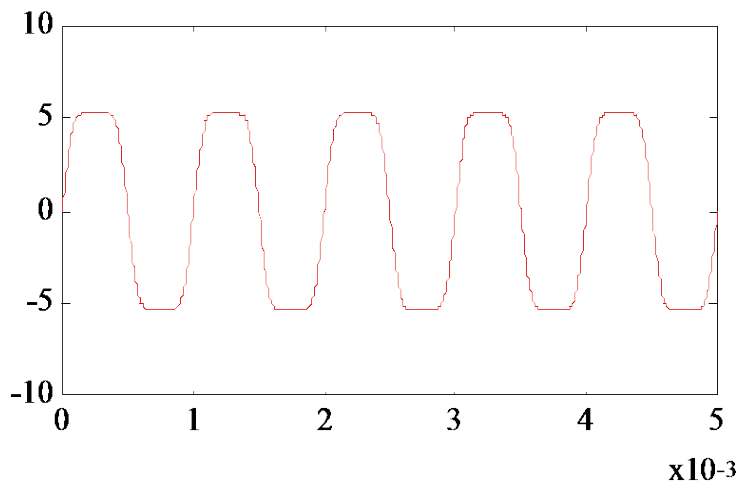

(d)

Solution 1.52

$$(a) 4700(1-.01) \leq R \leq 4700(1+.01) \quad \text{or} \quad 4650\Omega \leq R \leq 4750\Omega$$

$$(b) 4700(1-.05) \leq R \leq 4700(1+.05) \quad \text{or} \quad 4460\Omega \leq R \leq 4940\Omega$$

$$(c) 4700(1-.10) \leq R \leq 4700(1+.10) \quad \text{or} \quad 4230\Omega \leq R \leq 5170\Omega$$

Solution 1.53

$$10000\mu F(1-.5) \leq C \leq 10000\mu F(1+.2) \quad \text{or} \quad 5000\mu F \leq R \leq 12000\mu F$$

Solution 1.54

$$V_{nom} = 1.8V \quad |\Delta V| \leq 0.05V \quad T \leq \frac{0.05}{1.80} = 0.0278 \text{ or } 2.78 \%$$

Solution 1.55

$$8200(1-0.1) \leq R \leq 8200(1+0.1) \quad \text{or} \quad 7380\Omega \leq R \leq 9020\Omega$$

Yes, the resistor is within the allowable range of values.

Solution 1.56

(a) $5V(1-.05) \leq V \leq 5V(1+.05)$ or $4.75V \leq V \leq 5.25V$

$V = 5.30$ V exceeds the maximum range, so it is out of the specification limits.

(b) However, if the meter is reading 1.5% high, then the actual voltage would be

$$V_{meter} = 1.015V_{act} \quad \text{or} \quad V_{act} = \frac{5.30}{1.015} = 5.22V \quad \text{which is within specifications limits.}$$

Solution 1.57

$$TCR = \frac{\Delta R}{\Delta T} = \frac{6562 - 6066}{100 - 0} = 4.96 \frac{\Omega}{^{\circ}C}$$

$$R_{\text{nom}} = R|_{0^{\circ}C} + TCR (\Delta T) = 6066 + 4.96(27) = 6200\Omega$$

Solution 1.58

At 30°C, $7500\Omega(1-0.05) \leq R \leq 7500\Omega(1+0.05)$ or $7120\Omega \leq R \leq 7880\Omega$

Adding the effect of TC for $\Delta T = 45^\circ\text{C}$:

$$R_{\min} = 7120\Omega \left(1 + 45 \frac{2200}{10^6} \right) = 7820\Omega \quad R_{\max} = 7780\Omega \left[1 + 45(2.2 \times 10^{-3}) \right] = 8550\Omega$$

$7820\Omega \leq R \leq 8550\Omega$ with accumulated rounding

$7830\Omega \leq R \leq 8650\Omega$ more exact calculation

Solution 1.59

$I = 200 \mu\text{A}$, $R_1 = 150 \text{ k}\Omega$, $R_2 = 68 \text{ k}\Omega$ and $R_3 = 82 \text{ k}\Omega$.

$$I_1 = I \frac{R_2 + R_3}{R_1 + R_2 + R_3} = I \frac{1}{1 + \frac{R_1}{R_2 + R_3}} \quad \text{and similarly} \quad I_2 = I \frac{1}{1 + \frac{R_2 + R_3}{R_1}}$$

$$I_1^{\max} = \frac{200(1.02)}{1 + \frac{150\text{k}\Omega(0.90)}{68\text{k}\Omega(1.1) + 82\text{k}\Omega(1.1)}} \mu\text{A} = 112 \mu\text{A} \quad I_1^{\min} = \frac{200(0.98)}{1 + \frac{150\text{k}\Omega(1.1)}{68\text{k}\Omega(0.90) + 82\text{k}\Omega(0.90)}} \mu\text{A} = 88.2 \mu\text{A}$$

$$I_2^{\max} = \frac{200(1.02)}{1 + \frac{68\text{k}\Omega(0.90) + 82\text{k}\Omega(0.90)}{150\text{k}\Omega(1.1)}} \mu\text{A} = 112 \mu\text{A} \quad I_2^{\min} = \frac{200(0.98)}{1 + \frac{68\text{k}\Omega(1.1) + 82\text{k}\Omega(1.1)}{150\text{k}\Omega(0.90)}} \mu\text{A} = 88.2 \mu\text{A}$$

$$V_3 = I_2 R_3 = \frac{I}{\frac{1}{R_1} + \frac{1}{R_3} + \frac{R_2}{R_1 R_3}}$$

$$V_3^{\max} = \frac{200\mu\text{A}(1.02)}{\frac{1}{150\text{k}\Omega(1.1)} + \frac{1}{82\text{k}\Omega(1.1)} + \frac{68\text{k}\Omega(0.9)}{150\text{k}\Omega(1.1)(82\text{k}\Omega)(1.1)}} = 9.60 \text{ V}$$

$$V_3^{\min} = \frac{200\mu\text{A}(0.98)}{\frac{1}{150\text{k}\Omega(0.9)} + \frac{1}{82\text{k}\Omega(0.9)} + \frac{68\text{k}\Omega(1.1)}{150\text{k}\Omega(0.9)(82\text{k}\Omega)(0.9)}} = 6.89 \text{ V}$$

Solution 1.60

$V = 1 \text{ V}$, $R_1 = 24 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$ and $R_3 = 11 \text{ k}\Omega$.

$$\text{Let } R_X = R_2 \parallel R_3 \quad \text{then} \quad V_1 = V \frac{R_1}{R_1 + R_X} = \frac{V_1}{1 + \frac{R_X}{R_1}}$$

$$R_X^{\min} = \frac{30\text{k}\Omega(0.9)(11\text{k}\Omega)(0.9)}{30\text{k}\Omega(0.9) + 11\text{k}\Omega(0.9)} = 7.24\text{k}\Omega \quad R_X^{\max} = \frac{30\text{k}\Omega(1.1)(11\text{k}\Omega)(1.1)}{30\text{k}\Omega(1.1) + 11\text{k}\Omega(1.1)} = 8.85\text{k}\Omega$$

$$V_1^{\max} = \frac{1(1.05)}{1 + \frac{7.24\text{k}\Omega}{24\text{k}\Omega(1.1)}} = 0.824 \text{ V} \quad V_1^{\min} = \frac{1(0.95)}{1 + \frac{8.85\text{k}\Omega}{24\text{k}\Omega(0.9)}} = 0.674 \text{ V}$$

$$I_1 = \frac{V}{R_1 + R_X} \quad \text{and} \quad I_2 = I_1 \frac{R_3}{R_2 + R_3} = \left(\frac{V}{R_1 + R_X} \right) \frac{1}{1 + \frac{R_2}{R_3}}$$

$$I_2^{\max} = \frac{1(1.05)}{24\text{k}\Omega(0.9) + 7.24\text{k}\Omega} \frac{1}{1 + \frac{(30\text{k}\Omega)(0.9)}{11\text{k}\Omega(1.1)}} = 11.3 \mu\text{A}$$

$$I_2^{\min} = \frac{1(0.95)}{24\text{k}\Omega(1.1) + 8.85\text{k}\Omega} \frac{1}{1 + \frac{(30\text{k}\Omega)(1.1)}{11\text{k}\Omega(0.9)}} = 6.22 \mu\text{A}$$

$$I_3 = I_1 \frac{R_2}{R_2 + R_3} = \frac{I_1}{1 + \frac{R_3}{R_2}}$$

$$I_3^{\max} = \frac{1(1.05)}{24\text{k}\Omega(0.9) + 7.24\text{k}\Omega} \frac{1}{1 + \frac{(11\text{k}\Omega)(0.9)}{30\text{k}\Omega(1.1)}} = 28.0 \mu\text{A}$$

$$I_3^{\min} = \frac{1(0.95)}{24\text{k}\Omega(1.1) + 8.85\text{k}\Omega} \frac{1}{1 + \frac{(11\text{k}\Omega)(1.1)}{30\text{k}\Omega(0.9)}} = 18.6 \mu\text{A}$$

Solution 1.61

From Prob. 1.24: $R_{th} = \frac{1}{g_m + \frac{1}{R_1}}$

$$R_{th}^{\max} = \frac{1}{0.002(0.9) + \frac{1}{7.5 \times 10^4 (1.2)}} = 552 \, \Omega \quad R_{th}^{\min} = \frac{1}{0.002(1.1) + \frac{1}{7.5 \times 10^4 (0.8)}} = 451 \, \Omega$$

Solution 1.62

For one set of 200 cases using the Equations in Prob. 1.59 (mA & k Ω):

$$I = 0.200*(0.98 + 0.04* RAND()) \quad R_1 = 150*(0.9 + 0.2* RAND())$$

$$R_2 = 68*(0.9 + 0.2* RAND()) \quad R_3 = 82*(0.9 + 0.2* RAND())$$

	I ₁	I ₂	V ₃
Min	89.9 μ A	91.2 μ A	7.34 V
Max	110 μ A	109 μ A	9.23 V
Average	100 μ A	99.8 μ A	8.23 V

Solution 1.63

For one set of 200 cases using the equations in Prob. 1.60.

$$V = 1*(0.95 + 0.1* RAND()) \quad R_1 = 24000*(0.9 + 0.2* RAND())$$

$$R_2 = 30000*(0.9 + 0.2* RAND()) \quad R_3 = 11000*(0.9 + 0.2* RAND())$$

	V ₁	I ₂	I ₃
Min	0.685 V	6.70 μA	19.7 μA
Max	0.814V	10.1 μA	27.1 μA
Average	0.754 V	8.49 μA	22.9 μA

Solution 1.64

3.29, 0.995, -6.16; 3.295, 0.9952, -6.155

Solution 1.65

(a) $(1.763 \text{ mA})(20.70 \text{ k}\Omega) = 36.5 \text{ V}$ (b) 36 V

(c) $(0.1021 \text{ }\mu\text{A})(97.80 \text{ k}\Omega) = 9.99 \text{ V}; 10 \text{ V}$